
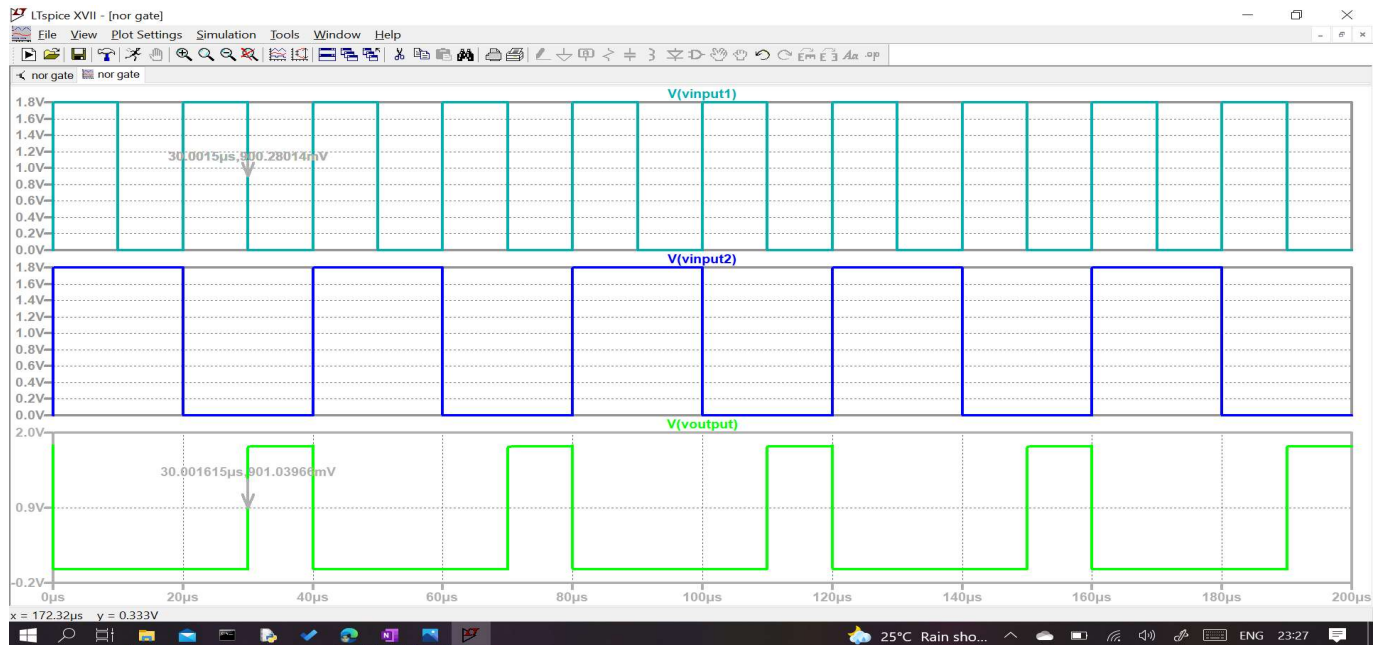


Assumptions Taken : 180nm Technology
 L=180nm, W=400nm(N-mos), W=800nm (P-mos)
 Input :Pulse Type & details are as Mentioned in the Diagram.

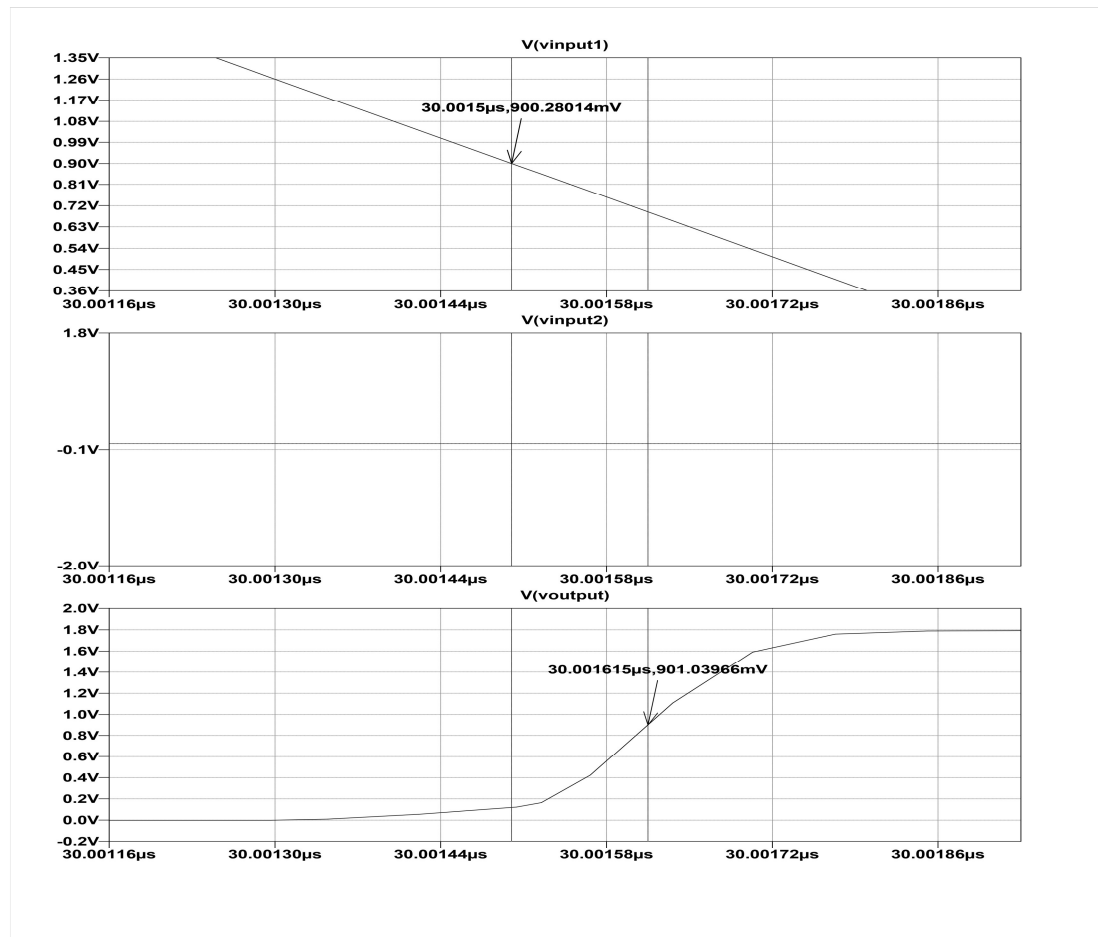BELOW ARE THE SWITCHING SIMULATIONS FOR CHANGING INPUT LOGIC :







Here Two Values are marked Which we can clearly see are marked at input crossing 50% of the value and the output crossing 50% of the value.

CALCULATIONS: $T_{\text{delay}} = 30.001615\mu\text{s} - 30.0015\mu\text{s} = 115 \text{ Pico seconds}$

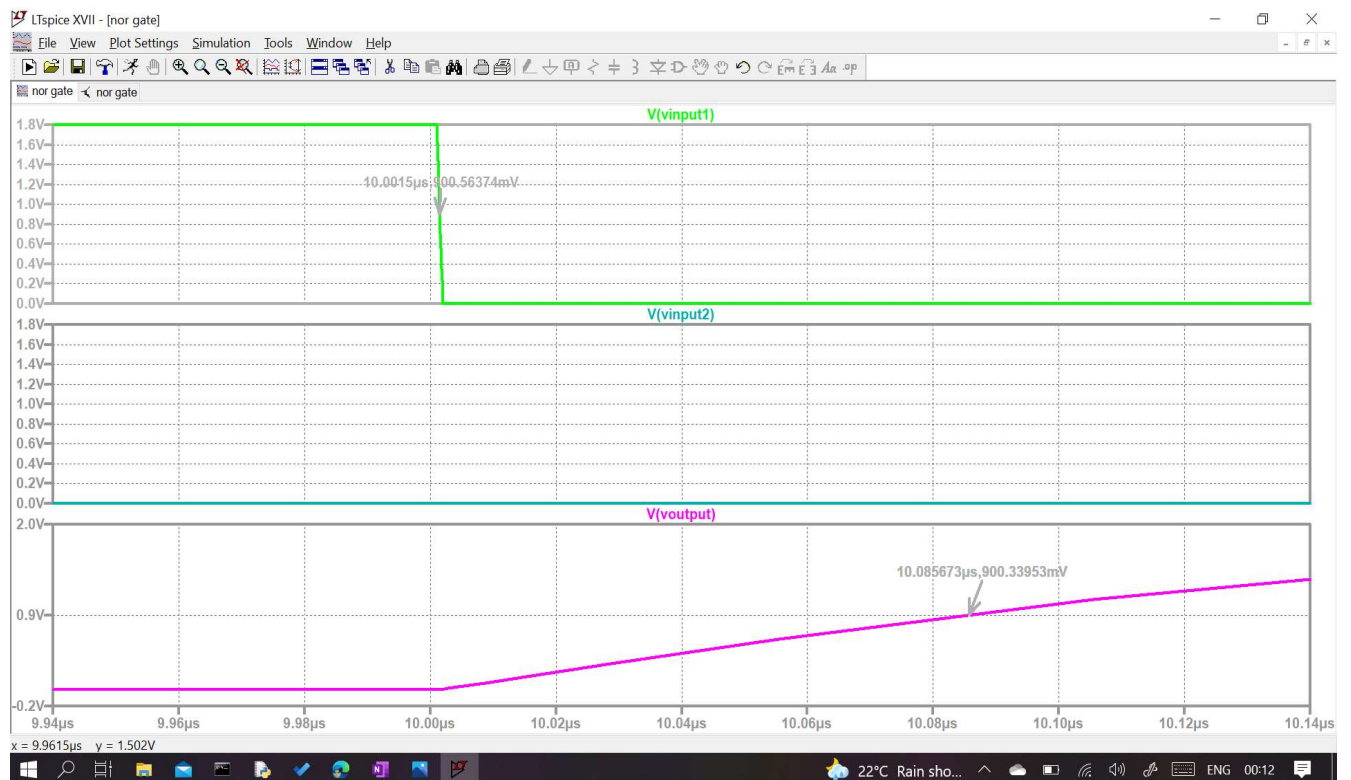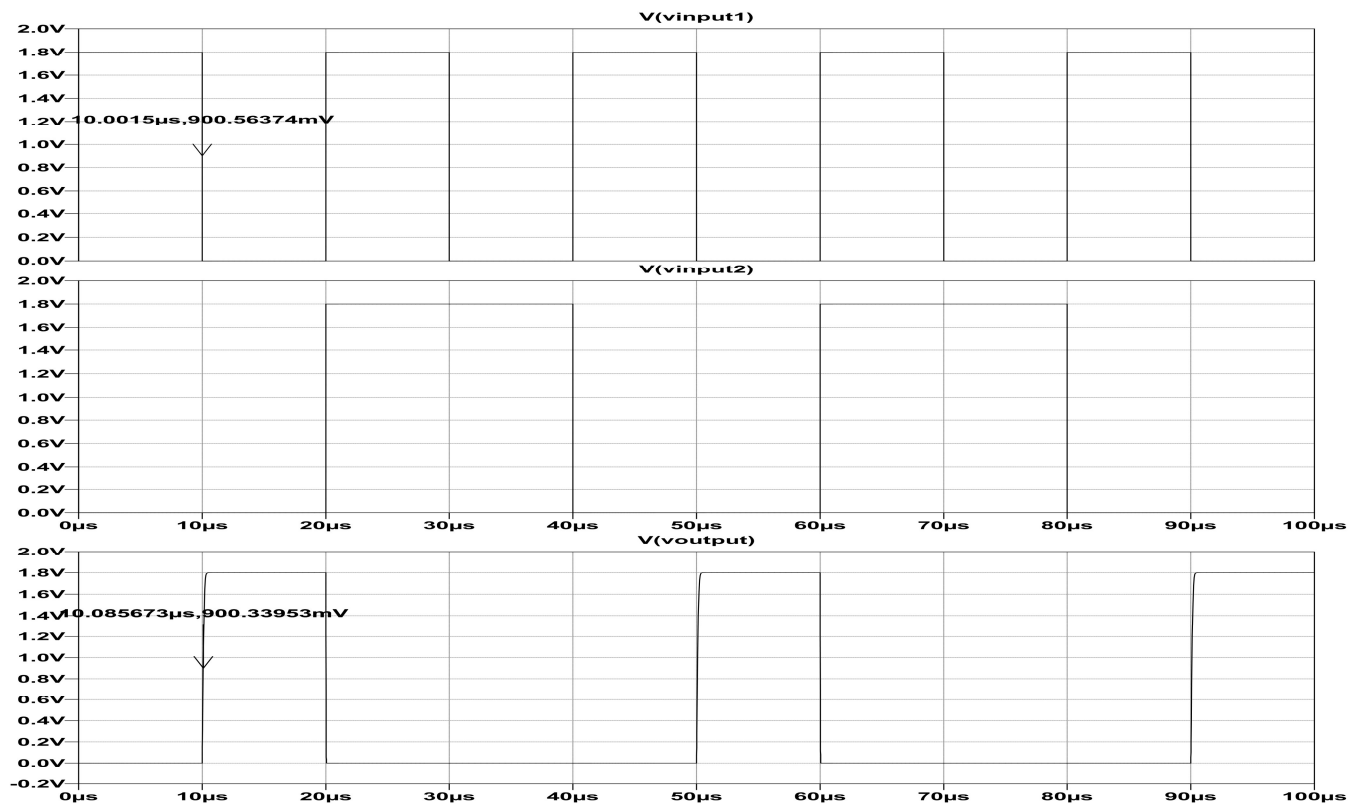With C load : Below Graphs Shows that the delay has increased by adding 10Pf Load at the output terminal.



These values are marked at Input Crossing of 50percent & the output crossing of 50 percent.

Calculations:

$T_{delay} = 10.08567\mu s - 10.0015\mu s = 84170 \text{ Pico seconds}$

Without C load : 115 Pico seconds

With C load : 84170 Pico seconds

Input 1	Input 2	Output	Delay Without Load	Delay With Load
Low (0)	Low(0)	High(1)	115 ps	84710 ps